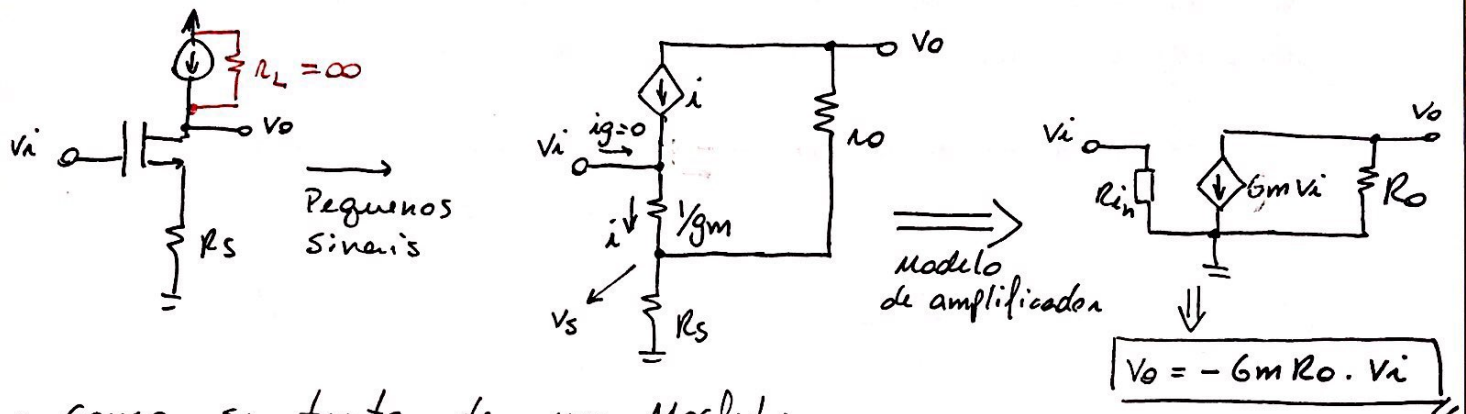


Nota de aula CEA

• Análise Amplificador CS com  $R_s$ :


① Modelagem amplificador de transcondutância:



• Como se trata de um Mosfet:

$R_{in} = \infty$

•  $R_o$  →

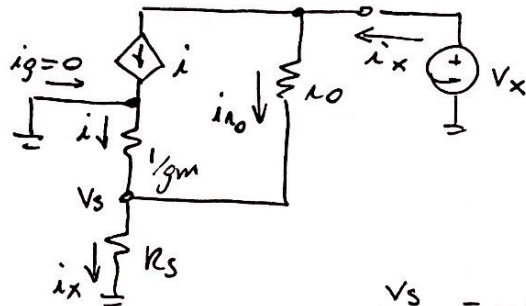

$$i_x = i + i_{ro}$$

$$i_x = V_s / R_s$$

$$i = -V_s / \frac{1}{g_m}$$

$$i_{ro} = \frac{V_x - V_s}{r_o}$$

$$\frac{V_s}{R_s} = -g_m V_s + \frac{V_x - V_s}{r_o}$$

$$\frac{V_x}{r_o} = V_s \left( \frac{1}{R_s} + \frac{1}{r_o} + g_m \right)$$

$$V_x = V_s \left( \frac{r_o + R_s + g_m R_s r_o}{R_s} \right)$$

$$V_s = \left[ \frac{R_s}{r_o + R_s + g_m R_s r_o} \right] \cdot V_x$$

$$i_x = \frac{V_s}{R_s} = \frac{V_x}{r_o + R_s + g_m R_s r_o}$$

$$R_o = \frac{V_x}{i_x} = r_o + R_s + g_m R_s r_o$$

→ se  $g_m r_o \gg 1$   $R_o \approx r_o (1 + g_m R_s)$

•  $G_m$

$$i_x = i + i_{ro} \rightarrow i_x = V_s / R_s ; i = \frac{V_i - V_s}{\frac{1}{g_m}} ; i_{ro} = \frac{-V_s}{r_o}$$

$$\frac{V_s}{R_s} = g_m (V_i - V_s) - \frac{V_s}{r_o} \Rightarrow V_s \left( \frac{1}{R_s} + \frac{1}{r_o} + g_m \right) = g_m V_i$$

$$V_s = \frac{g_m R_s r_o \cdot V_i}{R_s + r_o + g_m R_s r_o} \rightarrow i_x = \frac{V_s}{R_s} = \frac{g_m r_o \cdot V_i}{R_s + r_o + g_m R_s r_o}$$

$$G_m = \frac{i_x}{V_i} = \frac{g_m r_o}{R_s + r_o + g_m R_s r_o}$$

$$A_v = \frac{V_o}{V_i} = -G_m R_o = -g_m r_o$$

