
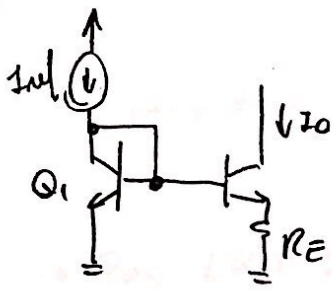



→ Espelho de Widlar → Cálculo de  $R_0$

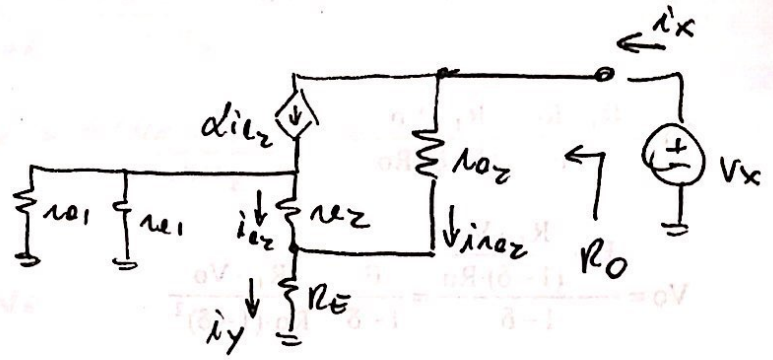

pequenas  
sinais.



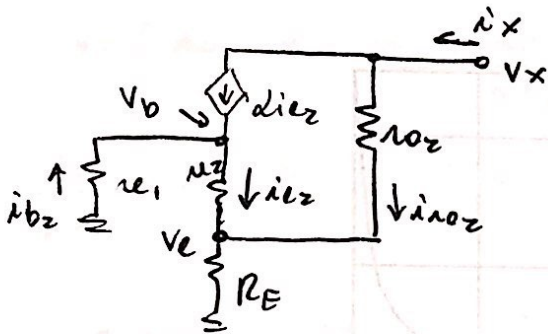Como  $r_{\pi 1} \gg r_{\pi 2} \rightarrow r_{\pi 1} // r_{\pi 2} \approx r_{\pi 2}$



$$\rightarrow i_x = \alpha i_{e2} + i_{\pi 2}$$

$$\frac{V_e}{R_E} = i_{e2} + i_{\pi 2}$$

$$(1) \frac{V_e}{R_E} = i_{e2} + i_x - \alpha i_{e2} = i_x + (1 - \alpha) i_{e2}$$

$$i_{e2} = \frac{V_b - V_e}{r_{\pi 2}} \rightarrow V_b = -i_{b2} r_{\pi 1} = -\frac{i_{e2} r_{\pi 1}}{\beta + 1}$$

$$i_{e2} = -\frac{i_{e2} r_{\pi 1}}{(\beta + 1) r_{\pi 2}} - \frac{V_e}{r_{\pi 2}} \rightarrow (\beta + 1) r_{\pi 2} = \frac{r_{\pi 1}}{\beta + 1}$$

$$i_{e2} \left( 1 + \frac{r_{\pi 1}}{\beta + 1} \right) = -\frac{V_e}{r_{\pi 2}}$$

$$(2) i_{e2} = \frac{-\frac{r_{\pi 1}}{\beta + 1}}{\frac{r_{\pi 1}}{\beta + 1} + r_{\pi 2}} \cdot \frac{V_e}{r_{\pi 2}} = \frac{-(\beta + 1)}{\beta + 1} \cdot \frac{V_e}{r_{\pi 2}}$$

→ substituindo (2) em (1)

$$\frac{V_e}{R_E} = i_x + (1 - \alpha) \cdot \frac{-(\beta + 1)}{\beta + 1} \cdot \frac{V_e}{r_{\pi 2}} \rightarrow 1 - \alpha = 1 - \frac{\beta}{\beta + 1} = \frac{1}{\beta + 1}$$

$$\frac{V_e}{R_E} = i_x - \frac{V_e}{\beta + 1} \rightarrow V_e \left( \frac{1}{R_E} + \frac{1}{\beta + 1} \right) = i_x$$

• Como  $\beta \gg 1$ , pois  $\beta \gg 1$

$$V_e \left( \frac{1}{R_E} + \frac{1}{\beta + 1} \right) = i_x \rightarrow \boxed{V_e = i_x (R_E // \beta + 1)}$$

• Continuando

$$i_{\lambda o_2} = i_x - \alpha i_{e_2} = i_x - \frac{\beta}{\beta+1} \left( \frac{-(\beta+1)}{\lambda_{\pi_2}} v_e \right)$$

$$i_{\lambda o_2} \approx i_x + \frac{\beta}{\lambda_{\pi_2}} v_e = i_x + \frac{\beta(R_E // \lambda_{\pi_2})}{\lambda_{\pi_2}} i_x$$

→ Por LKT:  $v_x = v_{\lambda o_2} + v_e$

$$v_x \approx \lambda_{o_2} \cdot i_{\lambda o_2} + (R_E // \lambda_{\pi_2}) i_x$$

$$v_x \approx \lambda_{o_2} i_x + \frac{\lambda_{o_2} \beta (R_E // \lambda_{\pi_2})}{\lambda_{\pi_2}} i_x + R_E // \lambda_{\pi_2} i_x$$

$$\frac{v_x}{i_x} = R_o \approx (R_E // \lambda_{\pi_2}) + \lambda_{o_2} + \frac{\beta \lambda_{o_2} (R_E // \lambda_{\pi_2})}{\lambda_{\pi_2}}$$

• mas,  $\lambda_{\pi_2} = \frac{V_T}{I_B} = \frac{\beta V_T}{I_C}$  e  $\frac{I_C}{V_T} = g_m$

logo,  $\lambda_{\pi_2} = \frac{\beta}{g_m}$

→ Assim:

$$R_o \approx (R_E // \lambda_{\pi_2}) + \lambda_{o_2} + g_m \lambda_{o_2} (R_E // \lambda_{\pi_2})$$

Se  $g_m \lambda_{o_2} \gg 1 \rightarrow \boxed{R_o \approx g_m \lambda_{o_2} (R_E // \lambda_{\pi_2})}$

ou  $R_o \approx (\lambda_{o_2} + g_m \lambda_{o_2} (R_E // \lambda_{\pi_2}))$   
 $= (1 + g_m (R_E // \lambda_{\pi_2})) \lambda_{o_2}$